

O módulo *Keyboard Reader* é constituído por três blocos principais: i) o decodificador de teclado (*Key Decode*); ii) o bloco de armazenamento (designado por *Ring Buffer*); e iii) o bloco de entrega ao consumidor (designado por *Output Buffer*). Neste caso o módulo *Control*, implementado em *software*, é a entidade consumidora.


 



Figura 1 – Diagrama de blocos do módulo *Keyboard Reader*

1 Key Decode

O bloco *Key Decode* implementa um decodificador de um teclado matricial 4x3 por *hardware*, sendo constituído por três sub-blocos: i) um teclado matricial de 4x3; ii) o bloco *Key Scan*, responsável pelo varrimento do teclado; e iii) o bloco *Key Control*, que realiza o controlo do varrimento e o controlo de fluxo, conforme o diagrama de blocos representado na Figura 2a. O controlo de fluxo de saída do bloco *Key Decode* (para o módulo *Ring Buffer*), define que o sinal K_{val} é ativado quando é detetada a pressão de uma tecla, sendo também disponibilizado o código dessa tecla no barramento $K_{0:3}$. Apenas é iniciado um novo ciclo de varrimento ao teclado quando o sinal K_{ack} for ativado e a tecla premida for libertada. O diagrama temporal do controlo de fluxo está representado na Figura 2b.

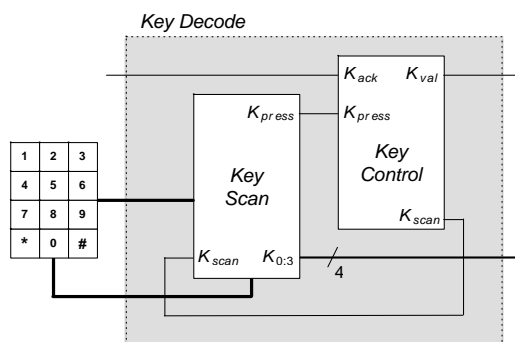

a) Diagrama de blocos

 

b) Diagrama temporal

Figura 2 – Bloco *Key Decode*

O bloco *Key Scan* foi implementado de acordo com o diagrama de blocos representado na Figura 3. Escolhemos a versão I pois foi a que o professor recomendou e ao longo do desenvolvimento do trabalho consideramos ser uma versão que nos agradou.

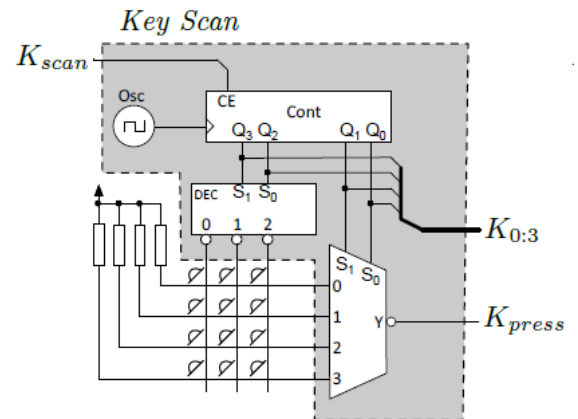


Figura 3 - Diagrama de blocos do bloco *Key Scan*

O bloco *Key Control* foi implementado pela máquina de estados representada em *ASM-chart* na Figura 4.

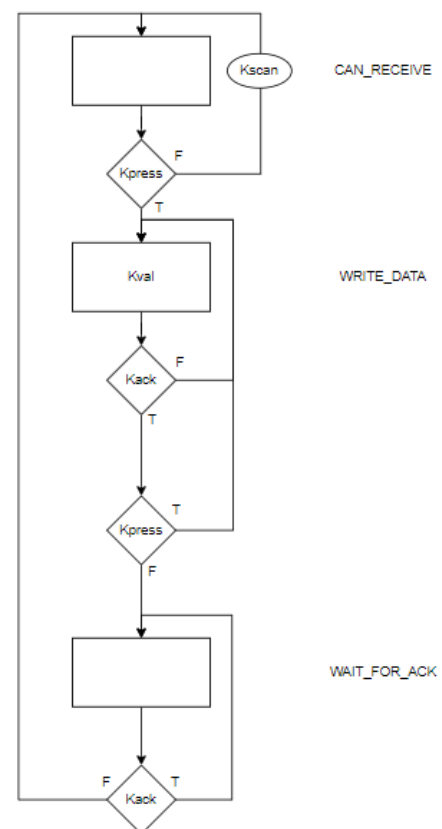


Figura 4 – Máquina de estados do bloco *Key Control*

A descrição hardware do bloco *Key Decode* em VHDL encontra-se no anexo D.

2 Interface com o *Control*

Implementou-se o módulo *Control* em *software*, recorrendo a linguagem *Kotlin* e seguindo a arquitetura lógica apresentada na Figura 5.

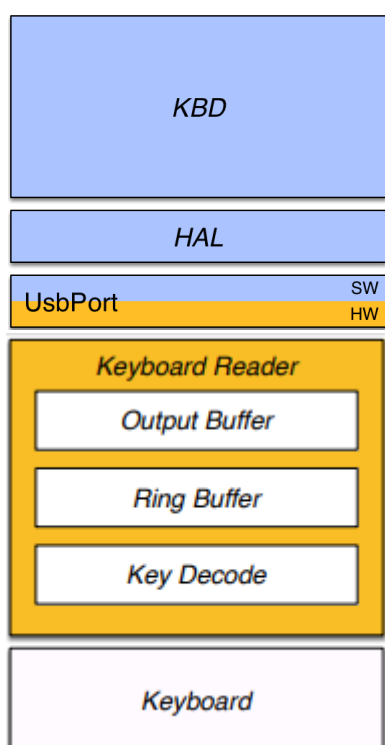


Figura 5 – Diagrama lógico do módulo *Control* de interface com o módulo *Keyboard Reader*

HAL e *KBD* desenvolvidos são descritos nas secções 2.1. e 2.2, e o código fonte desenvolvido nos Anexos O e P, respetivamente.

2.1 *HAL*

É a interação entre *usbPort* e o *software*. Desenvolvemos 6 funções:

2.1.1 *fun init()*

Inicia o *usbPort* a 0 e atualiza o *lastState* para 0.

2.1.2 *fun readBits()*

Lê o valor de output nos bits correspondentes a máscara enquanto restantes bits retornam a 0.

2.1.3 *fun isBits()*

Verifica o valor de um bit em específico.

2.1.4 *fun setBits()*

Coloca valores correspondentes a máscara a 1 e deixa os restantes como estavam.

2.1.5 *fun clrBits()*

Coloca valores correspondentes à máscara a 0 e deixa os restantes como estavam.

2.1.6 *fun writeBits()*

Tem como função escrever valor recebido nos bits indicados pela máscara (restantes bits mantêm-se).

A utilização da linha de código:

lastState = lastState.or(mask)

nas funções *setBits*, *clrBits* e *writeBits* serve para manter valor de *lastState* atualizado.

2.2 *KBD*

O desenvolvimento o *software* de *KBD* é composto por 3 funções:

2.2.1 *fun init()*

Inicia escrita e leitura do *usbPort* chamando o *HAL.init* e faz o *clearBits(HAL.clrBits)* à máscara do *Kack* (para este começar a 0).

2.2.2 *fun getKey()*

Lê o código da máscara que está no valor de cada tecla e transforma-o no devido caracter caso seja válida, é dado *ack* da tecla, espera tecla ser validada

e devolve o char correspondente á tecla que leu. Isto no caso de *Kval* estar ativo. Se *Kval* estiver inativo retorna NONE.

2.2.3 *fun waitKey()*

Recebe período (timeout) e tem um ciclo que tenta ler teclas. Se ler uma tecla válida retorna essa tecla. Se não, continua à procura até o tempo de o ciclo exceder e retorna NONE.

2.3 Ring Buffer

O bloco *Ring Buffer* desenvolvido é uma estrutura de dados para armazenamento de teclas com disciplina FIFO (*First*

In First Out), com capacidade de armazenar até oito palavras de quatro bits.

A escrita de dados no *Ring Buffer* inicia-se com a ativação do sinal DAV (*Data Available*) pelo sistema produtor, neste caso pelo *Key Decode*, indicando que tem dados para serem armazenados. Logo que tenha disponibilidade para armazenar informação, o *Ring Buffer* escreve os dados $D_{0:3}$ em memória. Concluída a escrita em memória ativa o sinal DAC (*Data Accepted*) para informar o sistema produtor que os dados foram aceites. O sistema produtor mantém o sinal DAV ativo até que DAC seja ativado. O *Ring Buffer* só desativa DAC depois de DAV ter sido desativado.

A implementação do *Ring Buffer* é baseada numa memória RAM (*Random Access Memory*). O endereço de escrita/leitura, selecionado por *putget*, é definido pelo bloco *Memory Address Control* (MAC) composto por dois registos, que contêm o endereço de escrita e leitura, designados por *putIndex* e *getIndex* respetivamente. O MAC suporta assim ações de *incPut* e *incGet*, gerando informação se a estrutura de dados está cheia (*full*) ou se está vazia (*empty*). O bloco *Ring Buffer* procede à entrega de dados à entidade consumidora, sempre que esta indique que está disponível para receber, através do sinal *Clear To Send* (CTS). Na Figura 6 é apresentado o diagrama de blocos para uma estrutura do bloco *Ring Buffer*.

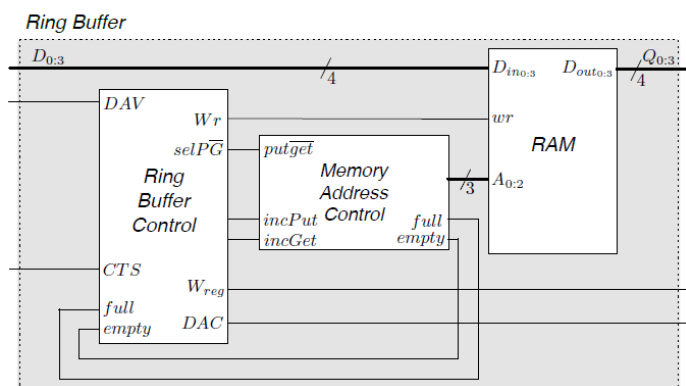
 


Figura 6 - Diagrama de blocos do bloco *Ring Buffer*

Figura 7 – Diagrama de blocos do bloco *Memory Address Control*

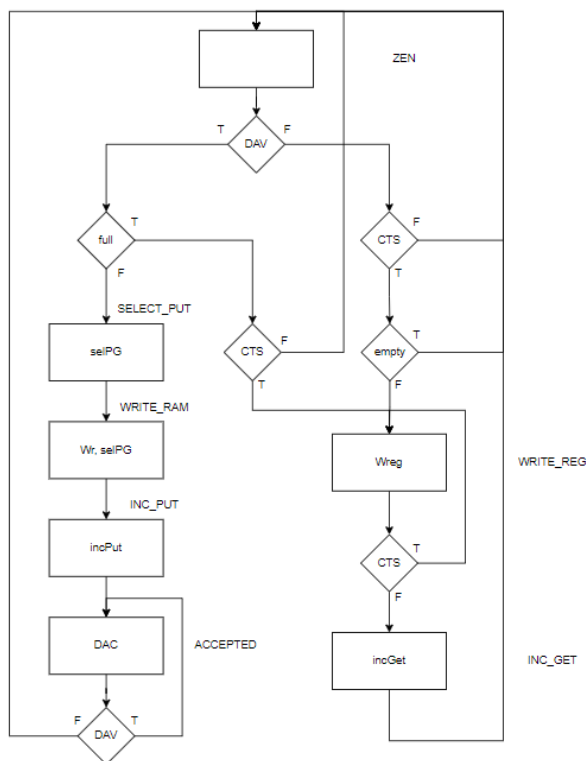


Figura 8 – Máquina de estados do *Ring Buffer Control*

2.4 Output Buffer

O bloco *Output Buffer* do *Keyboard Reader* é responsável pela interação com o sistema consumidor, neste caso o módulo *Control*.

O *Output Buffer* indica que está disponível para armazenar dados através do sinal *OBfree*. Assim, nesta situação o sistema produtor pode ativar o sinal *Load* para registrar os dados.

O *Control* quando pretende ler dados do *Output Buffer*, aguarda que o sinal *Dval* fique ativo, recolhe os dados e pulsa o sinal *ACK* indicando que estes já foram consumidos.

O *Output Buffer*, logo que o sinal *ACK* pulse, deve invalidar os dados baixando o sinal *Dval* e sinalizar que está novamente disponível para entregar dados ao sistema consumidor, ativando o sinal *OBfree*. Na Figura 9, é apresentado o diagrama de blocos do *Output Buffer*.

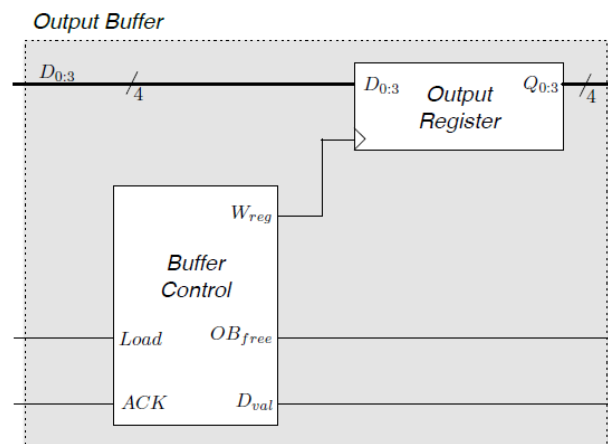


Figura 9 - Diagrama de blocos do bloco *Output Buffer*

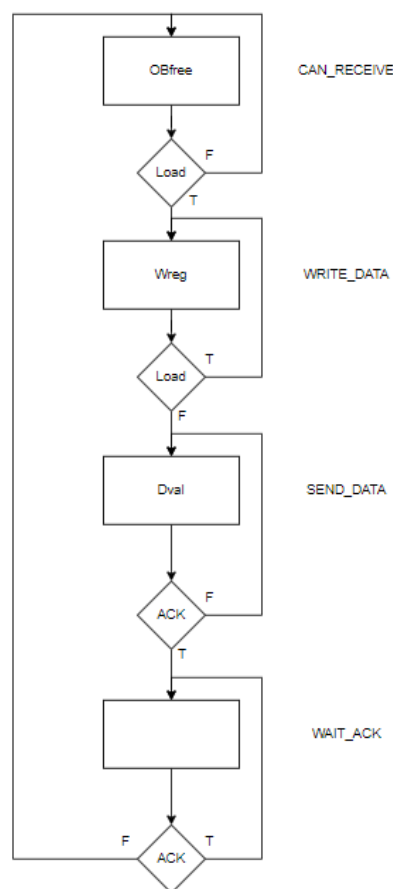


Figura 10 – Máquina de estados do *Buffer Control*

3 Conclusões

Por o clock da placa ser 50MHz, estava demasiado rápido para o propósito desejado, pelo que utilizámos o CLK_div com div = 1000, para que fosse mais lento e atingisse o objetivo.

A. Descrição VHDL do bloco Key Scan

```
library ieee;
use ieee.std_logic_1164.all;

entity KeyScan is
port(
  KScan, CLK, Reset: in std_logic;
  I : in std_logic_vector(3 downto 0);
  Kpress : out std_logic;
  O : out std_logic_vector(2 downto 0);
  K : out std_logic_vector(3 downto 0));
end KeyScan;

architecture arc_Keyscan of KeyScan is

  component Counter
  port(
    PL, CE, CLK, Reset: in std_logic;
    Data_in: in std_logic_vector(3 downto 0);
    TC: out std_logic;
    Q: out std_logic_vector(3 downto 0));
  end component;

  component Decoder
  port(
    S: in std_logic_vector(1 downto 0);
    O: out std_logic_vector(2 downto 0));
  end component;

  component MUX4x1
  port(
    S: in std_logic_vector(1 downto 0);
    I: in std_logic_vector(3 downto 0);
    Y: out std_logic);
  end component;

  signal kp : std_logic;
  signal col : std_logic_vector(2 downto 0);
  signal qcount : std_logic_vector(3 downto 0);

begin

  count: Counter port map(
    Reset => Reset,
    PL => '0',
    Data_in => "0000",
    CE => KScan,
    CLK => CLK,
    Q => qcount);
```

```
dec: Decoder port map(  
S(1) => qcount(3),  
S(0) => qcount(2),  
O => col);
```

```
mux: MUX4x1 port map(  
S(1) => qcount(1),  
S(0) => qcount(0),  
I => I,  
Y => kp);
```

```
O <= col;  
Kpress <= not kp;  
K <= qcount;
```

```
end arc_Keyscan;
```

B. Descrição VHDL do bloco *Key Control*

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity KeyControl is  
port(  
Kpress, Kack, CLK, Reset: in std_logic;  
Kval, Kscan: out std_logic);  
end KeyControl;
```

```
architecture arcKC of KeyControl is
```

```
type STATE_TYPE is (WAIT_FOR_PRESS, VALIDATE, WAIT_FOR_AFK);
```

```
signal CurrentState, NextState: STATE_TYPE;
```

```
begin
```

```
CurrentState <= WAIT_FOR_PRESS when Reset = '1' else NextState when rising_edge(CLK);
```

```
GenerateNextState:
```

```
process (CurrentState, Kpress, Kack)  
begin
```

```
    case CurrentState is
```

```
        when WAIT_FOR_PRESS =>
```

```
            if (Kpress = '1') then NextState <= VALIDATE;  
            else NextState <= WAIT_FOR_PRESS;  
            end if;
```

```
        when VALIDATE =>
```

```
            if (Kack = '1' and Kpress = '0') then NextState <= WAIT_FOR_AFK;  
            else NextState <= VALIDATE;  
            end if;
```

```
        when WAIT_FOR_AFK =>
```

```
            if (Kack = '0') then NextState <= WAIT_FOR_PRESS;  
            else NextState <= WAIT_FOR_AFK;  
            end if;
```

```
    end case;
```

```
end process;
```

```
Kval <= '1' when (CurrentState = VALIDATE) else '0';
```

```
Kscan <= '1' when (CurrentState = WAIT_FOR_PRESS and Kpress = '0') else '0';
```

end arcKC;

C. Descrição VHDL do bloco *CLK Div*

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.ALL;

entity CLKDIV is
generic(div: natural := 50000000);
port ( clk_in: in std_logic;
       clk_out: out std_logic);
end CLKDIV;

architecture bhv of CLKDIV is

signal count: integer:=1;
signal tmp : std_logic := '0';

begin

process(clk_in)
begin

    if(clk_in'event and clk_in='1') then
        count <= count+1;
        if (count = div/2) then
            tmp <= NOT tmp;
            count <= 1;
        end if;
    end if;
end process;

clk_out <= tmp;

End bhv;
```

D. Descrição VHDL do bloco *Key Decode*

```
library ieee;
use ieee.std_logic_1164.all;

entity KeyDecode is
port(
Kack , CLK, Reset: in std_logic;
I : in std_logic_vector(3 downto 0);
Kval : out std_logic;
O : out std_logic_vector(2 downto 0);
K : out std_logic_vector(3 downto 0));
end KeyDecode;
```

```
architecture arc_kd of KeyDecode is
  component CLKDIV
    generic(div: natural := 50000000);
    port ( clk_in: in std_logic;
           clk_out: out std_logic);
  end component;
```

```
  component KeyScan
    port(
      KScan, CLK, Reset: in std_logic;
      I : in std_logic_vector(3 downto 0);
      Kpress : out std_logic;
      O : out std_logic_vector(2 downto 0);
      K : out std_logic_vector(3 downto 0));
  end component;
```

```
  component KeyControl
    port(
      Kpress, Kack, CLK, Reset: in std_logic;
      Kval, Kscan: out std_logic);
  end component;
```

```
  signal kp, ks, clockm : std_logic;
```

```
begin
```

```
  clock: clkDIV generic map(1000)
  port map(
    clk_in => CLK,
    clk_out => clockm);
```

```
  scan : KeyScan port map(
    KScan => ks,
    CLK => clockm,
    Reset => Reset,
    I => I,
    Kpress => kp,
    O => O,
    K => K);
```

```
  control : KeyControl port map(
    Kpress => kp,
    Kack => Kack,
    CLK => clockm,
    Reset => Reset,
    Kval => Kval,
    KScan => ks);
```

```
end arc_kd;
```


E. Descrição VHDL do sub-bloco full add

```
library ieee;
use ieee.std_logic_1164.all;

entity full_add is
Port(A, B, Cin: in std_logic;
Cout, S: out std_logic);
end full_add;

architecture arc_fa of full_add is
begin
S <= A xor B xor Cin;
Cout <= (A and B) or (A and Cin) or (B and Cin);
end arc_fa;
```

F. Descrição VHDL do sub-bloco adder

```
library ieee;
use ieee.std_logic_1164.all;

entity adder is
Port(A, B :in std_logic_vector(3 downto 0);
Ci: in std_logic;
Co: out std_logic;
S: out std_logic_vector(3 downto 0));
end adder;

architecture arc_adder of adder is
component full_add
Port(A, B, Cin: in std_logic;
Cout, S: out std_logic);
end component;

signal c1, c2, c3: std_logic;

begin

fa1: full_add port map(
A => A(0),
B => B(0),
Cin => Ci,
S => S(0),
Cout => c1);

fa2: full_add port map(
A => A(1),
B => B(1),
Cin => c1,
S => S(1),
Cout => c2);

fa3: full_add port map(
A => A(2),
B => B(2),
Cin => c2,
S => S(2),
```

```
Cout => c3);

fa4: full_add port map(
A => A(3),
B => B(3),
Cin => C3,
S => S(3),
Cout => Co);

end arc_adder;
```

G. Descrição VHDL do sub-bloco Counter

```
library ieee;
use ieee.std_logic_1164.all;

-- CC -> contador crescente!
entity Counter is
port(
PL, CE, CLK, Reset: in std_logic;
Data_in: in std_logic_vector(3 downto 0);
TC: out std_logic;
Q: out std_logic_vector(3 downto 0));
end Counter;

architecture arc_cc of Counter is
component adder
Port(A, B :in std_logic_vector(3 downto 0);
Ci: in std_logic;
Co: out std_logic;
S: out std_logic_vector(3 downto 0));
end component;

component MUX2x1
port(A, B: in std_logic_vector(3 downto 0);
S: in std_logic;
Y: out std_logic_vector(3 downto 0));
end component;

component Registry
port(
D:in std_logic_vector(3 downto 0);
CLK, E, Reset: in std_logic;
Q: out std_logic_vector(3 downto 0));
end component;

component Terminal_Count
port(
Q : in std_logic_vector(3 downto 0);
TC: out std_logic);
end component;

signal outadder, outmux, outreg: std_logic_vector(3 downto 0);

begin

ad: adder port map(
A => outreg,
```

```
B => "0000",
Ci => CE,
S => outadder);

mux: MUX2x1 port map(
A => Data_in,
B => outadder,
S => PL,
Y => outmux);

reg: Registry port map(
Reset => Reset,
E => '1',
D => outmux,
CLK => CLK,
Q => outreg);

Q <= outreg;

utc: Terminal_Count port map(
Q => outreg,
TC => TC);

end arc_cc;
```

H. Descrição VHDL do sub-bloco MUX 2x1

```
library ieee;
use ieee.std_logic_1164.all;

entity MUX2x1 is
port(A, B: in std_logic_vector(3 downto 0);
S: in std_logic;
Y: out std_logic_vector(3 downto 0));
end MUX2x1;

architecture arc_mux of MUX2x1 is
begin
Y(0) <= (S and A(0)) or (not S and B(0));
Y(1) <= (S and A(1)) or (not S and B(1));
Y(2) <= (S and A(2)) or (not S and B(2));
Y(3) <= (S and A(3)) or (not S and B(3));
end arc_mux;
```

I. Descrição VHDL do sub-bloco Memory Address Control

```
library ieee;
use ieee.std_logic_1164.all;

entity MemoryAddressControl is
port(
putget, incPut, incGet, CLK, Reset : in std_logic;
full, empty : out std_logic;
A : out std_logic_vector(2 downto 0));
end MemoryAddressControl;

architecture arc of MemoryAddressControl is
```

```
component Counter
port(
  PL, CE, CLK, Reset: in std_logic;
  Data_in: in std_logic_vector(3 downto 0);
  TC: out std_logic;
  Q: out std_logic_vector(3 downto 0));
end component;

component Mux2x1
port(A, B: in std_logic_vector(3 downto 0);
  S: in std_logic;
  Y: out std_logic_vector(3 downto 0));
end component;

signal putIndex, getIndex, muxout : std_logic_vector(3 downto 0);
signal r, state_decider, equals : std_logic;

begin

--r <= Reset;
-- contador do indice no qual o put se encontra
incrementPut: Counter port map(
  PL => '0',--r,
  CE => incPut,
  CLK => CLK,
  Reset => Reset,
  Data_in => "0000",
  Q => putIndex);

-- contador do indice no qual o get se encontra
incrementGet: Counter port map(
  PL => '0',--r,
  CE => incGet,
  CLK => CLK,
  Reset => Reset,
  Data_in => "0000",
  Q => getIndex);

-- decide dependendo do sinal putget qual indice indicar como output
idxDecider : Mux2x1 port map(
  A => putIndex,
  B => getIndex,
  S => putget,
  Y => muxout);

A <= muxout(2 downto 0);

state_decider <= putIndex(3) xor getIndex(3);
equals <= (putIndex(2) xnor getIndex(2)) and (putIndex(1) xnor getIndex(1)) and (putIndex(0) xnor getIndex(0));
--caso os indices put e get sejam iguais, o quarto bit indica se a ram está vazia ou cheia,
--pela lógica de que se forem iguais quer dizer que está vazio e se forem diferentes, quer dizer
--que está cheio
empty <= not state_decider and equals;
full <= state_decider and equals;
end arc;
```

J. Descrição VHDL do sub-bloco Ring Buffer Control

```

library ieee;
use ieee.std_logic_1164.all;

entity RingBufferControl is
port(
  DAV, CTS, full, empty, Reset, CLK : in std_logic;
  Wr, selPG, Wreg, DAC, incPut, incGet : out std_logic);
end RingBufferControl;

architecture arc of RingBufferControl is

  type STATE_TYPE is (ZEN, SELECT_PUT, WRITE_RAM, INC_PUT, ACCEPTED, WRITE_REG, INC_GET);

  signal CurrentState, NextState: STATE_TYPE;

begin

  CurrentState <= ZEN when Reset = '1' else NextState when rising_edge(CLK);

  GenerateNextState:
  process(CurrentState, DAV, full, empty, CTS)
  begin
    case CurrentState is
      when ZEN =>
        if (DAV = '1' and full = '0') then NextState <= SELECT_PUT;
        elsif (DAV = '1' and full = '1' and CTS = '1') then NextState <= WRITE_REG;
        elsif (DAV = '0' and CTS = '1' and empty = '0') then NextState <= WRITE_REG;
        else NextState <= ZEN;
        end if;
      when SELECT_PUT => NextState <= WRITE_RAM;
      when WRITE_RAM => NextState <= INC_PUT;
      when INC_PUT => NextState <= ACCEPTED;
      when ACCEPTED =>
        if (DAV = '1') then NextState <= ACCEPTED;
        else NextState <= ZEN;
        end if;
      when WRITE_REG =>
        if (CTS = '1') then NextState <= WRITE_REG;
        else NextState <= INC_GET;
        end if;
      when INC_GET => NextState <= ZEN;
    end case;
  end process;

  selPG <= '1' when (CurrentState = SELECT_PUT or CurrentState = WRITE_RAM) else '0';
  Wr <= '1' when (CurrentState = WRITE_RAM) else '0';
  incPut <= '1' when (CurrentState = INC_PUT) else '0';
  DAC <= '1' when (CurrentState = ACCEPTED) else '0';
  Wreg <= '1' when (CurrentState = WRITE_REG) else '0';
  incGet <= '1' when (CurrentState = INC_GET) else '0';
end arc;

```

K. Descrição VHDL do bloco Ring Buffer

```

library ieee;
use ieee.std_logic_1164.all;

```

```
entity RingBuffer is
port(
  DAV, CTS, CLK, Reset : in std_logic;
  D : in std_logic_vector(3 downto 0);
  Wreg, DAC : out std_logic;
  Q : out std_logic_vector(3 downto 0));
end RingBuffer;

architecture arc of RingBuffer is
  component MemoryAddressControl
  port(
    putget, incPut, incGet, CLK, Reset : in std_logic;
    full, empty : out std_logic;
    A : out std_logic_vector(2 downto 0));
  end component;

  component RAM
  generic(
    ADDRESS_WIDTH : natural := 3;
    DATA_WIDTH : natural := 4
  );
  port(
    address : in std_logic_vector(ADDRESS_WIDTH - 1 downto 0);
    wr : in std_logic;
    din : in std_logic_vector(DATA_WIDTH - 1 downto 0);
    dout : out std_logic_vector(DATA_WIDTH - 1 downto 0));
  end component;

  component RingBufferControl
  port(
    DAV, CTS, full, empty, Reset, CLK : in std_logic;
    Wr, selPG, Wreg, DAC, incPut, incGet : out std_logic);
  end component;

  signal putget, incp, incg, f, e, wram : std_logic;
  signal idx : std_logic_vector(2 downto 0);

begin

  control : RingBufferControl port map(
    Reset => Reset,
    CLK => CLK,
    DAV => DAV,
    CTS => CTS,
    full => f,
    empty => e,
    Wr => wram,
    selPG => putget,
    Wreg => Wreg,
    DAC => DAC,
    incPut => incp,
    incGet => incg);

  mac : MemoryAddressControl port map(
    putget => putget,
    incPut => incp,
    incGet => incg,
```

```
CLK => CLK,  
Reset => Reset,  
full => f,  
empty => e,  
A => idx);
```

```
memory : RAM port map(  
address => idx(2 downto 0),  
wr => wram,  
din => D,  
dout => Q);  
end arc;
```

L. Descrição VHDL do sub-bloco Buffer Control

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity BufferControl is  
port(  
CLK, Reset, Load, ACK : in std_logic;  
Wreg, OBfree, Dval : out std_logic);  
end BufferControl;
```

```
architecture arc of BufferControl is
```

```
type STATE_TYPE is (CAN_RECEIVE, WRITE_DATA, SEND_DATA, WAIT_ACK);
```

```
signal CurrentState, NextState: STATE_TYPE;
```

```
begin
```

```
CurrentState <= CAN_RECEIVE when Reset = '1' else NextState when rising_edge(CLK);
```

```
GenerateNextState:  
process(Load, ACK)
```

```
begin
```

```
case CurrentState is
```

```
when CAN_RECEIVE =>
```

```
if (Load = '1') then NextState <= WRITE_DATA;
```

```
else NextState <= CAN_RECEIVE;
```

```
end if;
```

```
when WRITE_DATA =>
```

```
if (Load = '0') then NextState <= SEND_DATA;
```

```
else NextState <= WRITE_DATA;
```

```
end if;
```

```
when SEND_DATA =>
```

```
if (ACK = '0') then NextState <= SEND_DATA;
```

```
else NextState <= WAIT_ACK;
```

```
end if;
```

```
when WAIT_ACK =>
```

```
if(ACK = '1') then NextState <= WAIT_ACK;
```

```
else NextState <= CAN_RECEIVE;
```

```
end if;
```

```
end case;
```

```
end procesS;
```

```
OBfree <= '1' when (CurrentState = CAN_RECEIVE) else '0';  
Dval <= '1' when (CurrentState = SEND_DATA) else '0';  
Wreg <= '1' when (CurrentState = WRITE_DATA) else '0';  
end arc;
```

M.Descrição VHDL do sub-bloco *Output Buffer*

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity OutputBuffer is  
port(  
Load, ACK, CLK, Reset : in std_logic;  
D : in std_logic_vector(3 downto 0);  
OBfree, Dval : out std_logic;  
Q : out std_logic_vector(3 downto 0));  
end OutputBuffer;  
  
architecture arc of OutputBuffer is  
component BufferControl  
port(  
CLK, Reset, Load, ACK : in std_logic;  
Wreg, OBfree, Dval : out std_logic);  
end component;  
  
component Registry  
port(  
E, CLK, Reset : in std_logic;  
D : in std_logic_vector(3 downto 0);  
Q : out std_logic_vector(3 downto 0));  
end component;  
  
signal w : std_logic;  
  
begin  
  
control : BufferControl port map(  
CLK => CLK,  
Reset => Reset,  
Load => Load,  
ACK => ACK,  
Wreg => w,  
OBfree => OBfree,  
Dval => Dval);  
  
outreg : Registry port map(  
E => w,  
CLK => CLK,  
Reset => Reset,  
D => D,  
Q => Q);  
end arc;
```

N. Descrição VHDL do bloco *Keyboard Reader*

```
library ieee;  
use ieee.std_logic_1164.all;
```



```

entity KeyControl is
port(
  Kpress, Kack, CLK, Reset: in std_logic;
  Kval, Kscan: out std_logic);
end KeyControl;

architecture arcKC of KeyControl is

  type STATE_TYPE is (WAIT_FOR_PRESS, VALIDATE, WAIT_FOR_AFK);

  signal CurrentState, NextState: STATE_TYPE;

begin

  CurrentState <= WAIT_FOR_PRESS when Reset = '1' else NextState when rising_edge(CLK);

  GenerateNextState:
  process (CurrentState, Kpress, Kack)
  begin
    case CurrentState is
      when WAIT_FOR_PRESS =>
        if (Kpress = '1') then NextState <= VALIDATE;
        else NextState <= WAIT_FOR_PRESS;
        end if;
      when VALIDATE =>
        if (Kack = '1' and Kpress = '0') then NextState <= WAIT_FOR_AFK;
        else NextState <= VALIDATE;
        end if;
      when WAIT_FOR_AFK =>
        if (Kack = '0') then NextState <= WAIT_FOR_PRESS;
        else NextState <= WAIT_FOR_AFK;
        end if;
    end case;
  end process;

  Kval <= '1' when ( CurrentState = VALIDATE) else '0';
  Kscan <= '1' when ( CurrentState = WAIT_FOR_PRESS and Kpress = '0') else '0';

end arcKC;

```

O. Código Kotlin – HAL

```

import isel.leic.UsbPort

object HAL {
  private const val OFF = 0x00
  private const val INIT_STATE = 0x00
  private var lastState = INIT_STATE
  private var initialize = false

  // inicia o usbport a 0 e atualiza o lastState para 0
  fun init() {
    if (!initialize) {
      UsbPort.write(INIT_STATE)
      lastState = INIT_STATE
    }
  }
}

```

```
        initialize = true
    }
}

// le o(s) bit(s) indicado(s) na máscara
fun readBits(mask: Int) = UsbPort.read().and(mask)

// verifica se o bit indicado na máscara está on ou off
fun isBit(mask: Int) = UsbPort.read().and(mask) != OFF

// coloca o(s) bit(s) indicado(s) na máscara a on
fun setBits(mask: Int) {
    lastState = lastState.or(mask)
    UsbPort.write(lastState)
}

// coloca o(s) bit(s) indicado(s) na máscara a off
fun clrBits(mask: Int) {
    lastState = lastState.and(mask.inv())
    UsbPort.write(lastState)
}

// coloca o valor indicado em value no(s) bit(s) indicado(s) na máscara
fun writeBits(mask: Int, value: Int) {
    lastState = value.or(lastState.and(mask.inv()))
    UsbPort.write(lastState)
}
}
```

P. Código Kotlin - KBD

```
object KBD {
    private const val Kval = 0x01
    private const val Kack = 0x01
    private const val K = 0x1E
    const val waitTime = 2000L
    private const val sleepTime = 10L
    private const val CODE1 = 0x00
    private const val CODE2 = 0x04
    private const val CODE3 = 0x08
    private const val CODE4 = 0x01
    private const val CODE5 = 0x05
    private const val CODE6 = 0x09
    private const val CODE7 = 0x02
    private const val CODE8 = 0x06
    private const val CODE9 = 0x0A
    private const val CODE0 = 0x07
    private const val CODEEXT = 0x03
    private const val CODEHASH = 0x0B
}
```

```
// inicia o HAL e coloca o bit correspondente a K Ack a 0
fun init() {
    HAL.init()
    HAL.clrBits(Kack)
}

const val NONE = 0.toChar()

// le o que é escrito no teclado e devolve o que leu, caso não consiga ler nada devolve NONE
private fun getKey(): Int {
    if (HAL.isBit(Kval)) {
        val c = when (HAL.readBits(K).shr(1)) {
            CODE1 -> '1'.code
            CODE2 -> '2'.code
            CODE3 -> '3'.code
            CODE4 -> '4'.code
            CODE5 -> '5'.code
            CODE6 -> '6'.code
            CODE7 -> '7'.code
            CODE8 -> '8'.code
            CODE9 -> '9'.code
            CODEEXT -> '*'.code
            CODE0 -> '0'.code
            CODEHASH -> '#'.code
            else -> NONE.code
        }
        HAL.setBits(Kack)
        while (HAL.isBit(Kval)) {
            Thread.sleep(sleepTime)
        }
        HAL.clrBits(Kack)
        return c
    }
    return NONE.code
}

// chama o getKey() até passar o tempo de timeout ou até ler uma tecla
fun waitKey(timeout: Long): Int {
    val timeInit = System.currentTimeMillis()
    while (true) {
        val time = System.currentTimeMillis()
        val c = getKey()
        if (c != NONE.code) return c
        if (time - timeInit >= timeout) return NONE.code
    }
}
}
```