

O módulo de interface com o LCD (Serial LCD Interface, SLCDC) implementa a receção em série da informação enviada pelo módulo de controlo, entregando-a posteriormente ao LCD, conforme representado na Figura 1.

 


Figura 1 – Diagrama de blocos do Serial LCD Controller

1 SLCDC

O bloco Serial Receiver do SLCDC é constituído por três blocos principais: i) um bloco de controlo; ii) um contador de bits recebidos; e iii) um bloco conversor série paralelo, designados respetivamente por Serial Control, Counter, e Shift Register. O Serial Receiver deverá ser implementado com base no diagrama de blocos apresentado na Figura 2.

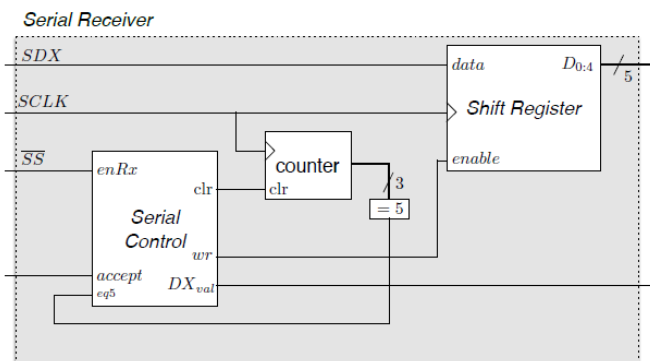


Figura 2 – Diagrama de blocos do Serial Receiver


 


Figura 3 – Diagrama de temporal do SLCDC

2 Interface com o Control

 Implementou-se o módulo *Control* em *software*, recorrendo a linguagem *Kotlin* e seguindo a arquitetura lógica




apresentada na Figura 4.

Figura 4 – Diagrama lógico do módulo *Control* de interface com o módulo *SLCDC*.

LCD e *Serial Emitter* desenvolvidos são descritos nas secções 2.1. e 2.2, e o código fonte desenvolvido nos Anexos P e Q, respetivamente.

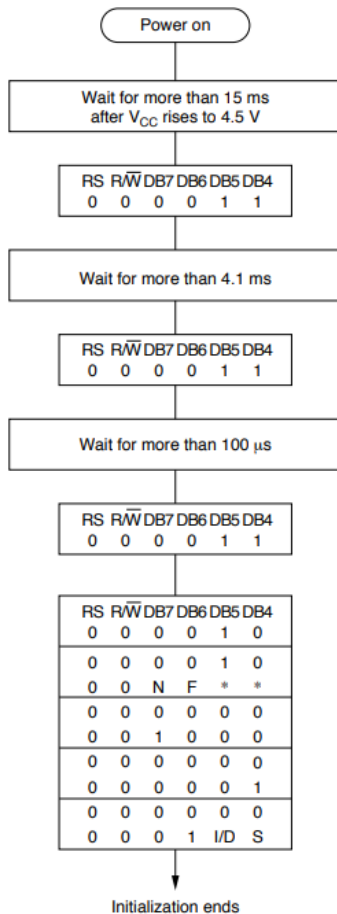2.1 LCD

Init que tem a seguinte sequência de comandos:



2.1.1 *fun writeNibbleSerial()*

c faz a transformação à *data* para incluir o valor do rs e chama a função *send* do serial emitter.

2.1.2 *fun writeNibble()*

apenas chama *writeNibbleSerial*.

fun writeByte()

divide a data de 8 bits em 2 nibbles, 4 bits da parte alta e 4 bits da parte baixa e chama o *writeNible* com cada uma das partes.

2.1.3 *fun writeCMD()*

chama *writeByte* indicando o rs a falso o que quer dizer que é um comando de LCD a executar.

2.1.4 *fun writeData()*

chama `writeByte` indicando que está a escrever data no display.

Cursor faz transformação de 2 ints para 1 int com a máscara correspondente à posição desejada.

2.2 *Serial Emitter*

Tem duas funções, o *init* e *send*.

No *init*, é chamado o `HAL.init`, e é chamado o `setBits` com a máscara `SS`, é `setBits` e não `clrBits` pois a variável `SS` é *active-low*.

No *send* em 1º lugar ativa o `SS` com `clrBits`, depois tem um ciclo no qual faz `clrBits` do `SCLOCK` divide a data que recebe bit a bit com `clrBits` ou `setBits` dependendo do valor e irá escrever isso em série ao invés de o escrever em paralelo.


Após isto coloca `SCLOCK` a 1 e faz 5 iterações. Depois do ciclo o *clock* é colocado a 0 e negamos o `SS` e fazemos um *sleep* de 1ms para que a placa consiga receber a informação antes de passar para a próxima trama.

3 *Conclusões*


Software envia tramas mais rápido do que LCD consegue receber então colocamos um “*sleep*” de 1ms para que a placa consiga receber a informação antes de passar para a próxima trama.

A. Máquinas de estado

a. LCDDispatcher

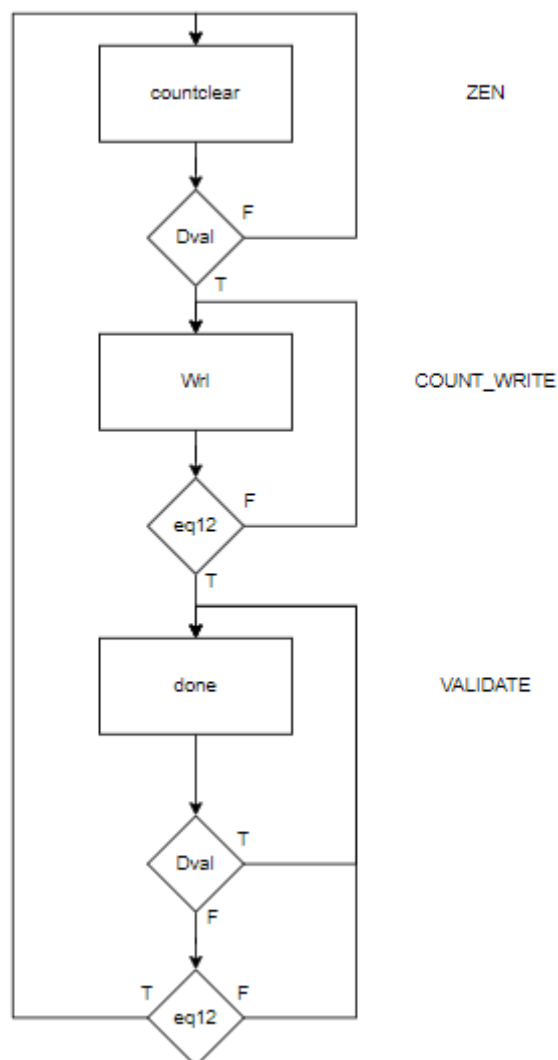

b. SerialControl

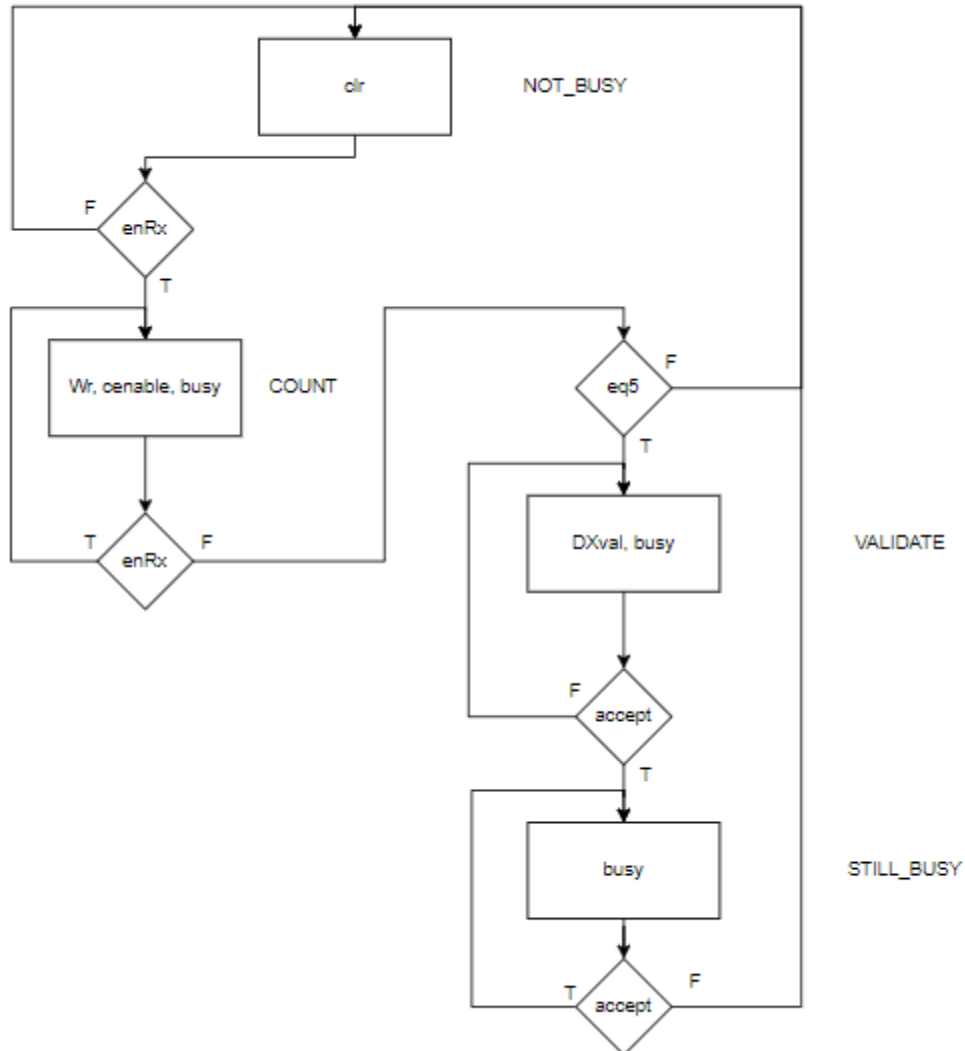

B. Atribuição de pinos do módulo *SLCDC*

```
set_global_assignment -name TOP_LEVEL_ENTITY "DE10_Lite"
set_global_assignment -name DEVICE_FILTER_PACKAGE FBGA
set_global_assignment -name SDC_FILE DE10_Lite.sdc
set_global_assignment -name INTERNAL_FLASH_UPDATE_MODE "SINGLE IMAGE WITH ERAM"

# clock
set_location_assignment PIN_P11 -to CLK

# inputs
set_location_assignment PIN_C10 -to Reset
#set_location_assignment PIN_C11 -to accept

# Leds
set_location_assignment PIN_A8 -to Dout[0]
set_location_assignment PIN_A9 -to Dout[1]
set_location_assignment PIN_A10 -to Dout[2]
set_location_assignment PIN_B10 -to Dout[3]
set_location_assignment PIN_D13 -to Dout[4]
set_location_assignment PIN_B11 -to Wrl
```

C. Descrição em VHDL do bloco *SLCDC*

```
library ieee;
use ieee.std_logic_1164.all;

entity SLCDC is
port(
SS, SCLK, CLK, SDX, Reset : in std_logic;
Wrl : out std_logic;
Dout : out std_logic_vector(4 downto 0));
end SLCDC;

architecture arc_slcdc of SLCDC is
component SerialReceiver
port(
SS, SCLK, CLK, SDX, accept, Reset : in std_logic;
DXval : out std_logic;
D : out std_logic_vector(4 downto 0));
end component;

component LCDDispatcher
port(
Dval, CLK, Reset : in std_logic;
```

```
Din : in std_logic_vector(4 downto 0);
Wrl, done : out std_logic;
Dout : out std_logic_vector(4 downto 0));
end component;

signal state, v : std_logic;
signal d : std_logic_vector(4 downto 0);

begin

sr : SerialReceiver port map(
CLK => CLK,
Reset => Reset,
SS => SS,
SCLK => SCLK,
SDX => SDX,
accept => state,
DXval => v,
D => d);

lcdd : LCDDispatcher port map(
Reset => Reset,
CLK => CLK,
Dval => v,
Din => d,
Wrl => Wrl,
done => state,
Dout => Dout);

end arc_slcdc;
```

D. Descrição em VHDL do sub-bloco Serial Receiver

```
library ieee;
use ieee.std_logic_1164.all;

entity SerialReceiver is
port(
SS, SCLK, CLK, SDX, accept, Reset : in std_logic;
DXval, busy : out std_logic;
D : out std_logic_vector(4 downto 0));
end SerialReceiver;

architecture arc_sr of SerialReceiver is
component SerialControl
port(
Reset, enRx, accept, eq5, CLK : in std_logic;
clr, wr, DXval, cenable, busy : out std_logic);
end component;

component ShiftRegister
port(
data, clk, enable, reset : in std_logic;
D : out std_logic_vector(4 downto 0));
end component;
```

```

component Counter
port(
  PL, CE, CLK, Reset: in std_logic;
  Data_in: in std_logic_vector(3 downto 0);
  TC: out std_logic;
  Q: out std_logic_vector(3 downto 0));
end component;

signal count : std_logic_vector(3 downto 0);
signal equal, clear, enwr, cenable : std_logic;

begin

c : Counter port map(
  Reset => clear,
  PL => '0',
  CE => cenable,
  CLK => SCLK,
  Data_in => "0000",
  Q => count);

equal <= '1' when (count(2) = '1' and count(1) = '0' and count(0) = '1') else '0';

sc : SerialControl port map(
  busy => busy,
  Reset => Reset,
  CLK => CLK,
  enRx => SS,
  accept => accept,
  eq5 => equal,
  clr => clear,
  cenable => cenable,
  wr => enwr,
  DXval => DXval);

sr : ShiftRegister port map(
  reset => '0',
  data => SDX,
  clk => SCLK,
  enable => enwr,
  D => D);

end arc_sr;

```

E. Descrição em VHDL do sub-bloco Shift Register

```

library ieee;
use ieee.std_logic_1164.all;

entity ShiftRegister is
port(
  data, clk, enable, reset : in std_logic;
  D : out std_logic_vector(4 downto 0));
end ShiftRegister;

architecture arc_sr of ShiftRegister is

```



```
component FFD
PORT( CLK : in std_logic;
      RESET : in STD_LOGIC;
      SET : in std_logic;
      D : IN STD_LOGIC;
      EN : IN STD_LOGIC;
      Q : out std_logic
    );
end component;
```

```
signal f1, f2, f3, f4: std_logic;
```

```
begin
```

```
ffd4: FFD port map(
  SET => '0',
  RESET => reset,
  CLK => clk,
  D => data,
  EN => enable,
  Q => f4);
```

```
ffd3: FFD port map(
  SET => '0',
  RESET => reset,
  CLK => clk,
  D => f4,
  EN => enable,
  Q => f3);
```

```
ffd2: FFD port map(
  SET => '0',
  RESET => reset,
  CLK => clk,
  D => f3,
  EN => enable,
  Q => f2);
```

```
ffd1: FFD port map(
  SET => '0',
  RESET => reset,
  CLK => clk,
  D => f2,
  EN => enable,
  Q => f1);
```

```
ffd0: FFD port map(
  SET => '0',
  RESET => reset,
  CLK => clk,
  D => f1,
  EN => enable,
  Q => D(0));
```

```
D(1) <= f1;
D(2) <= f2;
D(3) <= f3;
```

D(4) <= f4;

end arc_sr;

F. Descrição em VHDL do sub-bloco Serial Control

library ieee;

use ieee.std_logic_1164.all;

entity SerialControl is

port(

Reset, enRx, accept, eq5, CLK : in std_logic;

clr, wr, DXval, cenable, busy : out std_logic);

end SerialControl;

architecture arc_sc of SerialControl is

type STATE_TYPE is (NOT_BUSY, COUNT, VALIDATE, STILL_BUSY);

signal CurrentState, NextState: STATE_TYPE;

begin

CurrentState <= NOT_BUSY when Reset = '1' else NextState when rising_edge(CLK);

GenerateNextState:

process(CurrentState, enRx, eq5, accept)

begin

case CurrentState is

when NOT_BUSY =>

if (enRx = '0') then NextState <= COUNT;

else NextState <= NOT_BUSY;

end if;

when COUNT =>

if (enRx = '1') then

if (eq5 = '1') then NextState <= VALIDATE;

else NextState <= NOT_BUSY;

end if;

else NextState <= COUNT;

end if;

when VALIDATE =>

if (accept = '1') then NextState <= STILL_BUSY;

else NextState <= VALIDATE;

end if;

when STILL_BUSY =>

if (accept = '0') then NextState <= NOT_BUSY;

else NextState <= STILL_BUSY;

end if;

end case;

end process;

clr <= '1' when (CurrentState = NOT_BUSY) else '0';

cenable <= '1' when (CurrentState = COUNT) else '0';

wr <= '1' when (CurrentState = COUNT) else '0';

DXval <= '1' when (CurrentState = VALIDATE) else '0';

busy <= '0' when (CurrentState = NOT_BUSY) else '1';

end arc_sc;

G. Descrição em VHDL do sub-bloco Dispatcher

```
library ieee;
use ieee.std_logic_1164.all;

entity Dispatcher is
port(
Dval, Reset, CLK, eq12 : in std_logic;
Wrl, done, countclear : out std_logic);
end Dispatcher;

architecture arc of Dispatcher is
type STATE_TYPE is (ZEN, COUNT_WRITE, VALIDATE);

signal CurrentState, NextState: STATE_TYPE;
signal equal : std_logic;

begin

CurrentState <= ZEN when Reset = '1' else NextState when rising_edge(CLK);
equal <= eq12;

GenerateNextState:
process(CurrentState, Dval, equal)
begin
    case CurrentState is
        when ZEN =>
            if (Dval = '1') then NextState <= COUNT_WRITE;
            else NextState <= ZEN;
            end if;
        when COUNT_WRITE =>
            if (equal = '1') then NextState <= VALIDATE;
            else NextState <= COUNT_WRITE;
            end if;
        when VALIDATE =>
            if (Dval = '0' and equal = '1') then NextState <= ZEN;
            else NextState <= VALIDATE;
            end if;
    end case;
end process;

Wrl <= '1' when (CurrentState = COUNT_WRITE) else '0';
done <= '1' when (CurrentState = VALIDATE) else '0';
countclear <= '1' when (CurrentState = ZEN) else '0';
end arc;
```

H. Descrição em VHDL do sub-bloco Terminal Count

```
library ieee;
use ieee.std_logic_1164.all;

entity Terminal_Count is
```

```
port(  
  Q : in std_logic_vector(3 downto 0);  
  TC: out std_logic);  
end Terminal_Count;  
  
architecture arc_tc of Terminal_Count is  
begin  
  TC <= Q(0) and Q(1) and Q(2) and Q(3);  
end arc_tc;
```

I. Descrição em VHDL do sub-bloco Registry

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity Registry is  
port(  
  D:in std_logic_vector(3 downto 0);  
  CLK, E, Reset: in std_logic;  
  Q: out std_logic_vector(3 downto 0));  
end Registry;  
  
architecture arc_reg of Registry is  
  component FFD  
  port(  
    CLK : in std_logic;  
    RESET : in std_logic;  
    SET : in std_logic;  
    D : in std_logic;  
    EN : in std_logic;  
    Q : out std_logic  
  );  
end component;  
  
begin  
  
  ff0: FFD port map(  
    SET => '0',  
    RESET => Reset,  
    CLK => CLK,  
    D => D(0),  
    EN => E,  
    Q => Q(0));  
  
  ff1: FFD port map(  
    SET => '0',  
    RESET => Reset,  
    CLK => CLK,  
    D => D(1),  
    EN => E,  
    Q => Q(1));  
  
  ff2: FFD port map(  
    SET => '0',  
    RESET => Reset,  
    CLK => CLK,  
    D => D(2),  
    EN => E,  
    Q => Q(2));
```

```
ff3: FFD port map(  
SET => '0',  
RESET => Reset,  
CLK => CLK,  
D => D(3),  
EN => E,  
Q => Q(3));  
  
end arc_reg;
```

J. Descrição em VHDL do sub-bloco FFD

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY FFD IS  
PORT( CLK : in std_logic;  
      RESET : in STD_LOGIC;  
      SET : in std_logic;  
      D : IN STD_LOGIC;  
      EN : IN STD_LOGIC;  
      Q : out std_logic  
      );  
END FFD;  
  
ARCHITECTURE LogicFunction OF FFD IS  
  
BEGIN  
  
Q <= '0' when RESET = '1' else '1' when SET = '1' else D WHEN rising_edge(clk) and EN = '1';  
  
END LogicFunction;
```

K. Descrição em VHDL do sub-bloco LCDDispatcher

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity LCDDispatcher is  
port(  
Dval, Reset, CLK : in std_logic;  
Din : in std_logic_vector(4 downto 0);  
Wrl, done : out std_logic;  
Dout : out std_logic_vector(4 downto 0));  
end LCDDispatcher;
```

```

architecture arc_lcdd of LCDDispatcher is
  component Dispatcher
    port(
      Dval, Reset, CLK, eq12 : in std_logic;
      Wrl, done, countclear : out std_logic);
  end component;

  component Counter
    port(
      PL, CE, CLK, Reset: in std_logic;
      Data_in: in std_logic_vector(3 downto 0);
      TC: out std_logic;
      Q: out std_logic_vector(3 downto 0));
  end component;

  signal eq12, countclear, cenable, wr, d, clean: std_logic;
  signal count: std_logic_vector(3 downto 0);

begin

  disp: Dispatcher port map(
    Dval => Dval,
    Reset => Reset,
    CLK => CLK,
    eq12 => eq12,
    Wrl => wr,
    done => d,
    countclear => countclear);

  cup: Counter port map(
    Reset => Reset,
    PL => clean,
    CE => cenable,
    CLK => CLK,
    Data_in => "0000",
    Q => count);

  clean <= eq12 or countclear;
  Wrl <= wr;
  eq12 <= count(3) and count(2) and not count(1) and not count(0);
  done <= d;
  Dout <= Din;
  cenable <= wr or d;

end arc_lcdd;

```

L. Descrição em VHDL do sub-bloco Counter

```

library ieee;
use ieee.std_logic_1164.all;

-- CC -> contador crescente!
entity Counter is
  port(

```

```
PL, CE, CLK, Reset: in std_logic;
Data_in: in std_logic_vector(3 downto 0);
TC: out std_logic;
Q: out std_logic_vector(3 downto 0));
end Counter;

architecture arc_cc of Counter is
component adder
Port(A, B :in std_logic_vector(3 downto 0);
Ci: in std_logic;
Co: out std_logic;
S: out std_logic_vector(3 downto 0));
end component;

component MUX2x1
port(A, B: in std_logic_vector(3 downto 0);
S: in std_logic;
Y: out std_logic_vector(3 downto 0));
end component;

component Registry
port(
D:in std_logic_vector(3 downto 0);
CLK, E, Reset: in std_logic;
Q: out std_logic_vector(3 downto 0));
end component;

component Terminal_Count
port(
Q : in std_logic_vector(3 downto 0);
TC: out std_logic);
end component;

signal outadder, outmux, outreg: std_logic_vector(3 downto 0);

begin

ad: adder port map(
A => outreg,
B => "0000",
Ci => CE,
S => outadder);

mux: MUX2x1 port map(
A => Data_in,
B => outadder,
S => PL,
Y => outmux);

reg: Registry port map(
Reset => Reset,
E => '1',
D => outmux,
CLK => CLK,
Q => outreg);

Q <= outreg;
```

```
utc: Terminal_Count port map(  
Q => outreg,  
TC => TC);  
  
end arc_cc;
```

M.Descrição em VHDL do sub-bloco adder

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity adder is  
Port(A, B :in std_logic_vector(3 downto 0);  
Ci: in std_logic;  
Co: out std_logic;  
S: out std_logic_vector(3 downto 0));  
end adder;  
  
architecture arc_adder of adder is  
component full_add  
Port(A, B, Cin: in std_logic;  
Cout, S: out std_logic);  
end component;  
  
signal c1, c2, c3: std_logic;  
  
begin  
  
fa1: full_add port map(  
A => A(0),  
B => B(0),  
Cin => Ci,  
S => S(0),  
Cout => c1);  
  
fa2: full_add port map(  
A => A(1),  
B => B(1),  
Cin => C1,  
S => S(1),  
Cout => c2);  
  
fa3: full_add port map(  
A => A(2),  
B => B(2),  
Cin => C2,  
S => S(2),  
Cout => c3);  
  
fa4: full_add port map(  
A => A(3),  
B => B(3),  
Cin => C3,  
S => S(3),  
Cout => Co);  
  
end arc_adder;
```


N. Descrição em VHDL do sub-bloco full add

```
library ieee;
use ieee.std_logic_1164.all;

entity full_add is
Port(A, B, Cin: in std_logic;
Cout, S: out std_logic);
end full_add;

architecture arc_fa of full_add is
begin
S <= A xor B xor Cin;
Cout <= (A and B) or (A and Cin) or (B and Cin);
end arc_fa;
```

O. Descrição em VHDL do sub-bloco MUX 2x1

```
library ieee;
use ieee.std_logic_1164.all;

entity MUX2x1 is
port(A, B: in std_logic_vector(3 downto 0);
S: in std_logic;
Y: out std_logic_vector(3 downto 0));
end MUX2x1;

architecture arc_mux of MUX2x1 is
begin
Y(0)<=(S and A(0)) or (not S and B(0));
Y(1)<=(S and A(1)) or (not S and B(1));
Y(2)<=(S and A(2)) or (not S and B(2));
Y(3)<=(S and A(3)) or (not S and B(3));
end arc_mux;
```

P. Código Kotlin – LCD

```
object LCD {
    private const val RS = 0x04
    private const val Enable = 0x02
    private const val DATA = 0x78
    private const val LOW = 0x0F
    private const val SLEEPTIME = 1L
    private const val SLEEPTIME1 = 40L
    private const val SLEEPTIME2 = 5L
    private const val SLEEPWRITE = 40
    private const val SLEEPSET = 230
    private const val SLEEPCLR = 270
    private const val ON = 0x01
    private const val OFF = 0x00
    private const val SET8BITS = 0x03
```

```
private const val SET4BITS = 0x02
private const val NUM_LINES_CHAR = 0x28
private const val DISPLAY_OFF = 0x08
private const val DISPLAY_CLEAR = 0x01
private const val ENTRY_MODE = 0x06
private const val DISPLAY_ON_CONTROL = 0x0E
private const val SERIAL = true

// Escreve um nibble de comando/dados no LCD em paralelo
private fun writeNibbleParallel(rs: Boolean, data: Int) {
    HAL.writeBits(RS, (if (rs) ON else OFF).shl(2))
    HAL.writeBits(DATA, data.shl(3))
    Thread.sleep(0, SLEEPWRITE)
    HAL.setBits(Enable)
    Thread.sleep(0, SLEEPSET)
    HAL.clrBits(Enable)
    Thread.sleep(0, SLEEPCLR)
}

// Escreve um nibble de comando/dados no LCD em série
private fun writeNibbleSerial(rs: Boolean, data: Int) {
    val r = if (rs) ON else OFF
    SerialEmitter.send(SerialEmitter.Destination.LCD, data.shl(1) + r)
}

// Escreve um nibble de comando/dados no LCD
private fun writeNibble(rs: Boolean, data: Int) {
    if (SERIAL) writeNibbleSerial(rs, data) else writeNibbleParallel(rs, data)
}

// Escreve um byte de comando/dados no LCD
private fun writeByte(rs: Boolean, data: Int) {
    writeNibble(rs, data.shr(4))
    writeNibble(rs, data.and(LOW))
}

// Escreve um comando no LCD
private fun writeCMD(data: Int) {
    writeByte(false, data)
}

// Escreve um dado no LCD
private fun writeDATA(data: Int) {
    writeByte(true, data)
}

// Envia a sequência de iniciação para comunicação a 4 bits.
fun init() {
    SerialEmitter.init()
    Thread.sleep(SLEEPTIME1)
    writeNibble(false, SET8BITS)
    Thread.sleep(SLEEPTIME2)
```

```

writeNibble(false, SET8BITS)
Thread.sleep(SLEEPTIME)
writeNibble(false, SET8BITS)
Thread.sleep(SLEEPTIME)
writeNibble(false, SET4BITS)
Thread.sleep(SLEEPTIME)
writeCMD(NUM_LINES_CHAR)
Thread.sleep(SLEEPTIME)
writeCMD(DISPLAY_OFF)
Thread.sleep(SLEEPTIME)
writeCMD(DISPLAY_CLEAR)
Thread.sleep(SLEEPTIME)
writeCMD(ENTRY_MODE)
Thread.sleep(SLEEPTIME)
writeCMD(DISPLAY_ON_CONTROL)
}

// Escreve um carácter na posição corrente.
fun write(c: Char) {
    writeDATA(c.code)
    Thread.sleep(50)
}

// Escreve uma "string" na posição corrente.
fun write(text: String) {
    text.forEach { write(it) }
}

// Envia comando para posicionar cursor ('line':0..LINES-1 , 'column':0..COLS-1)
fun cursor(line: Int, column: Int) {
    writeByte(false, (line * 4 + 8) * 16 + column)
}

// Envia comando para limpar o ecrã e posicionar o cursor em (0,0)
fun clear() {
    writeCMD(DISPLAY_CLEAR)
}

```

Q. Código Kotlin – SerialEmitter

```

object SerialEmitter {

    enum class Destination { LCD, DOOR }

    private const val SLEEPTIME = 1L
    private const val SSLCD = 0x02
    private const val SDX = 0x04
    private const val SCLOCK = 0x08
    private const val SSDOOR = 0x10
    private const val busy = 0x20
    private const val MAX_LENGTH = 5
    private const val OFF = 0x00

```

```
// inicia o HAL e coloca os bits relativos ao SS tanto do lcd como da door a 1 (pois são active low)
fun init() {
    HAL.init()
    HAL.setBits(SSLCD)
    HAL.setBits(SSDOOR)
}

// escreve 5 bits de informação, 1 a 1, no usbport
fun send(addr: Destination, data: Int) {
    val mask = if (addr == Destination.DOOR) SSDOOR else SSLCD
    HAL.clrBits(mask)
    for (i in 0 until MAX_LENGTH) {
        HAL.clrBits(SCLOCK)
        val b = data.and(1.shl(i))
        if (b == OFF) {
            HAL.clrBits(SDX)
        } else {
            HAL.setBits(SDX)
        }
        HAL.setBits(SCLOCK)
    }
    HAL.clrBits(SCLOCK)
    HAL.setBits(mask)
    Thread.sleep(SLEEPTIME)
}

// verifica a condição do sinal busy
fun isBusy() = HAL.isBit(busy)
}
```